
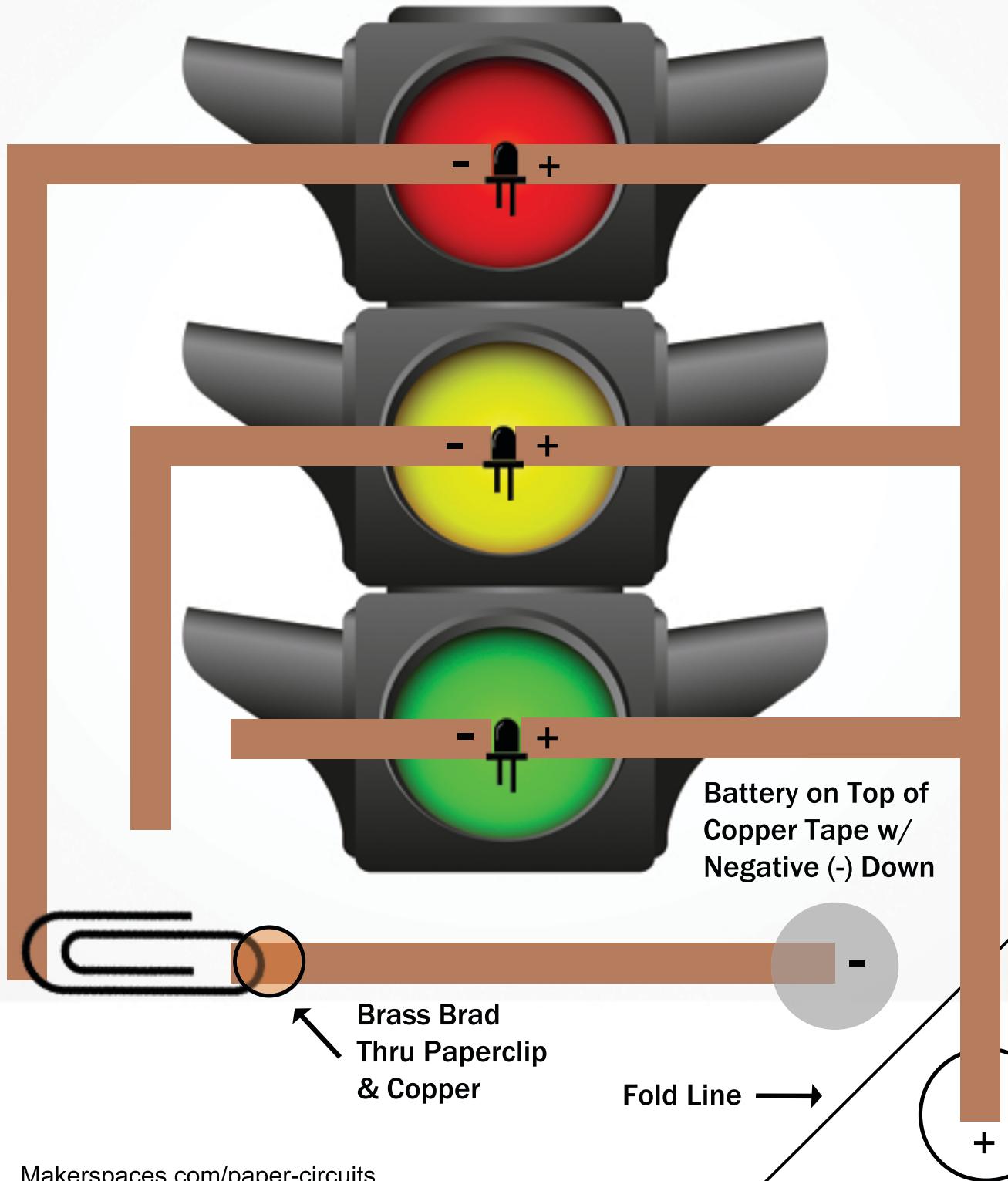



Traffic Lights

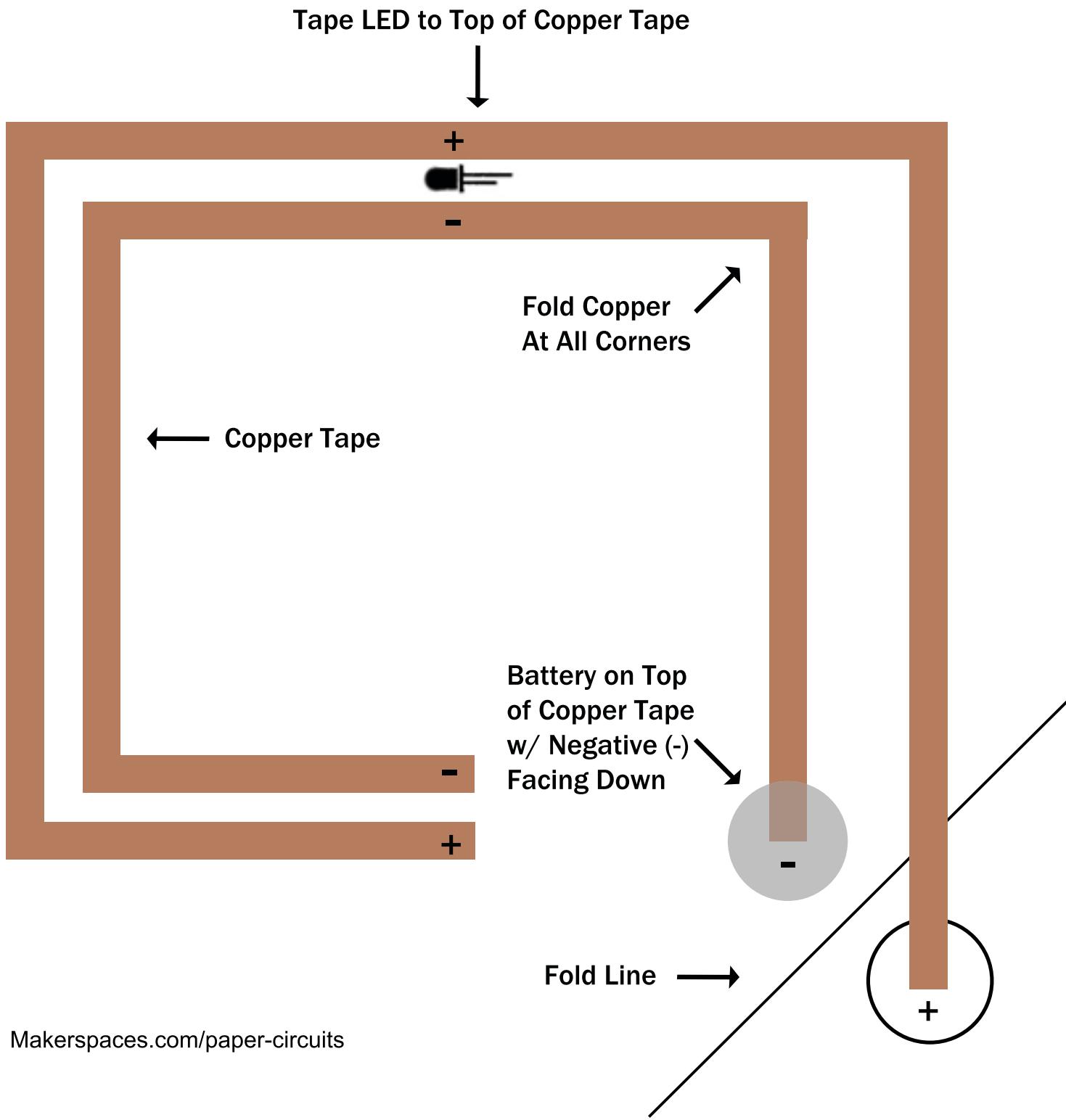

Parallel Circuit



Doorbell Circuit

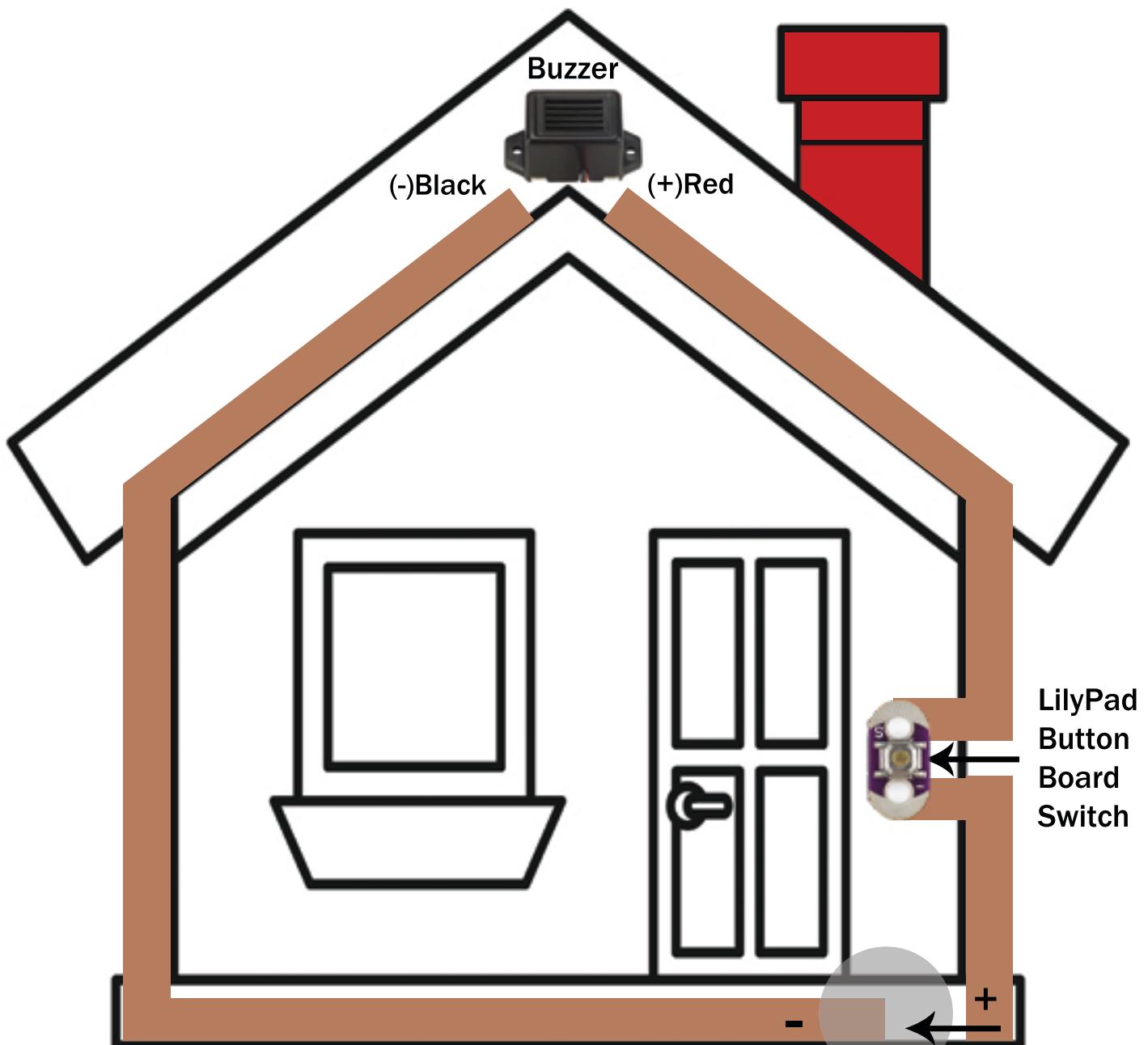


Color in this house
to make it a home.

Battery on Top
of Copper Tape
w/ Negative (-)
Facing Down

Copper Tape
on Top of
Battery (+)

Flap/Tab Switch

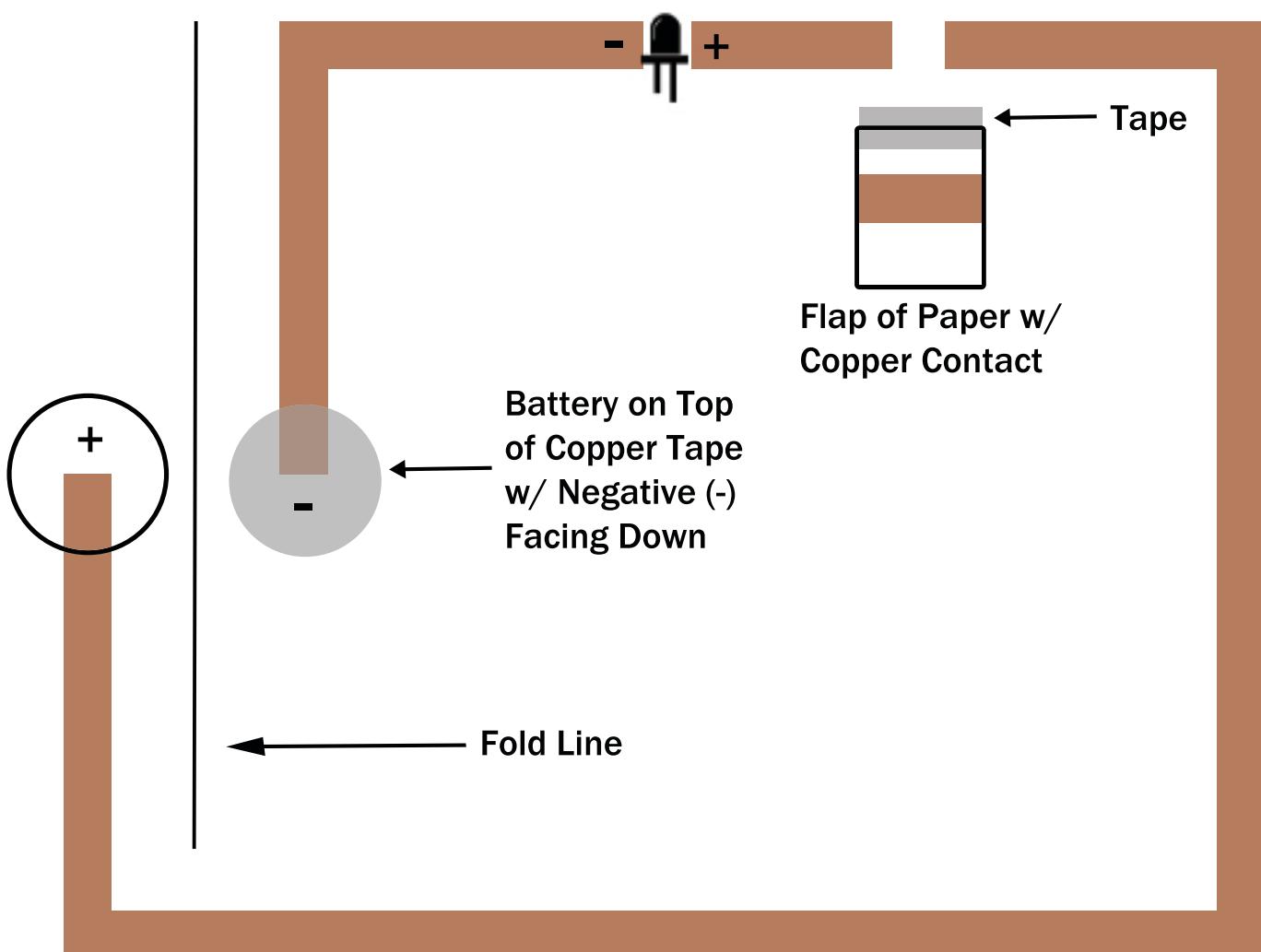

Desk Lamp

